



D.Y. PATIL INTERNATIONAL UNIVERSITY
B.TECH CSE FY SEM-2
A.Y. 2022-2023

Name: Suryakant Upadhyay

PRN: 20220802043

Subject: DIGITAL LOGIC AND DESIGN

Batch: A1

EXPERIMENT-3 (A)

Aim:

Design and implement Code converter- Binary to Gray.

Requirements:

NI LabVIEW tool

Theory:

Binary Code:

A symbolic representation of data/ information is called code. The base or radix of the binary number is 2. Hence, it has two independent symbols. The symbols used are 0 and 1. A binary digit is called as a bit. A binary number consists of sequence of bits, each of which is either a 0 or 1. Each bit carries a weight based on its position relative to the binary point. The weight of each bit position is one power of 2 greater than the weight of the position to its immediate right. e. g. of binary number is 100011 which is equivalent to decimal number 35.

BCD CODE:

Numeric codes represent numeric information i.e. only numbers as a series of 0's and 1's. Numeric codes used to represent decimal digits are called Binary Coded Decimal (BCD) codes. A BCD code is one, in which the digits of a decimal number are encoded-one at a time into group of four binary digits. There are a large number of BCD codes in order to represent decimal digits 0, 1, 2, ..., 9, it is necessary to use a sequence of at least four binary digits. Such a sequence of binary digits which represents a decimal digit is called code word.

Gray Code:

It is a non-weighted code; therefore, it is not suitable for arithmetic operations. It is a cyclic code because successive code words in this code differ in one bit position only i.e. it is a unit distance code.

Circuit Diagram:

Circuit Diagram

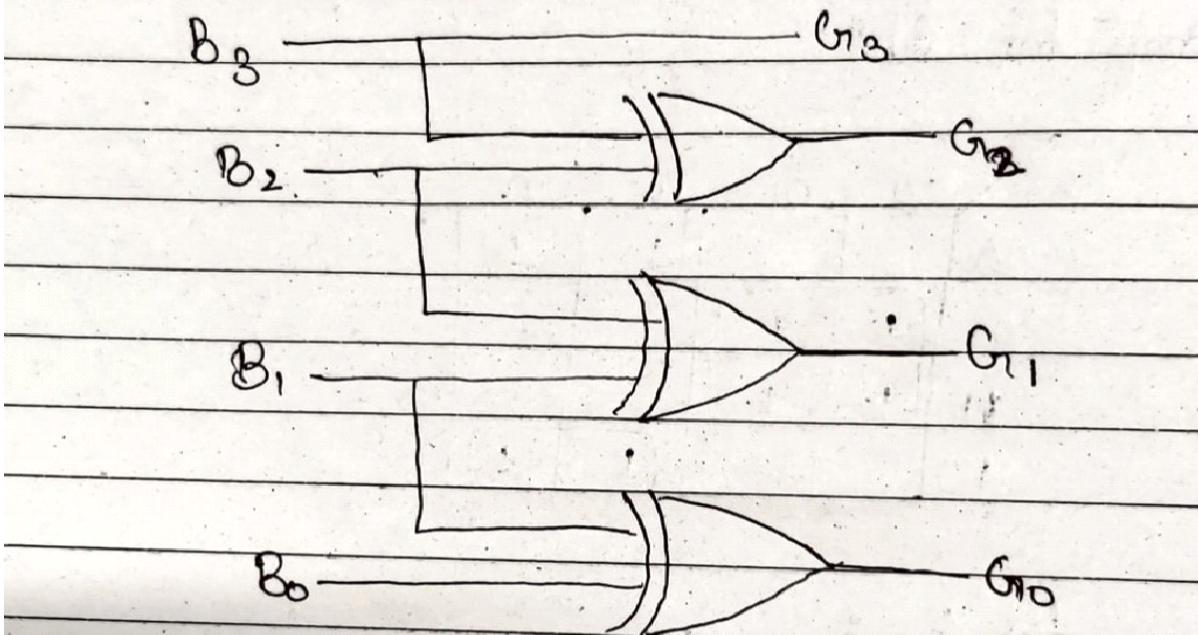


Fig : Binary to Gray converter.

Mathematical equation.

$$G_{10} = B_0 B_1' + B_1 B_0' = B_0 \oplus B_1$$

$$G_{11} = B_1 \oplus B_2$$

$$G_{12} = B_2 \oplus B_3$$

$$G_{13} = B_3$$

K-map for G_0 :

	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

K-map for G_1 :

	00	01	11	10
00			1	1
01	1	1		
11	1	1		
10			1	1

K-map for G_2 :

	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

K-map for G_3 :

	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

Observation Table:

Input Variables- B_3, B_2, B_1, B_0



Output Variables- G_3, G_2, G_1, G_0


Where B_3, B_2, B_1, B_0 represents the binary bits,

G_3, G_2, G_1, G_0 represents the gray code bits of binary number.

Input (Binary Code)				Output (Gray Code)			
B_3	B_2	B_1	B_0	G_3	G_2	G_1	G_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	0	0	1
0	1	1	1	0	0	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	1	1	0
1	1	0	1	1	1	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

Output:

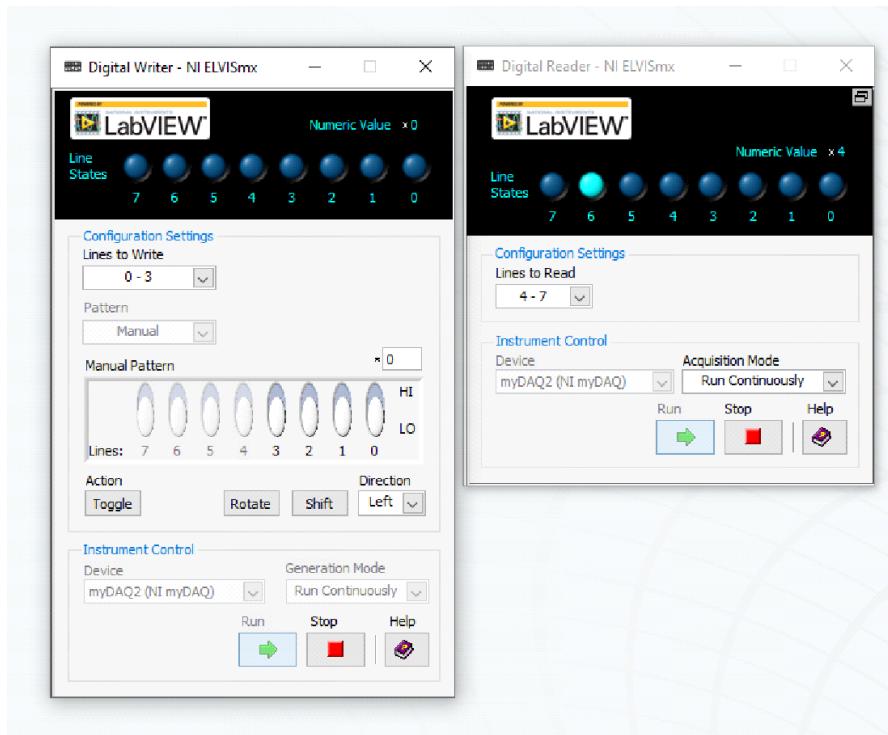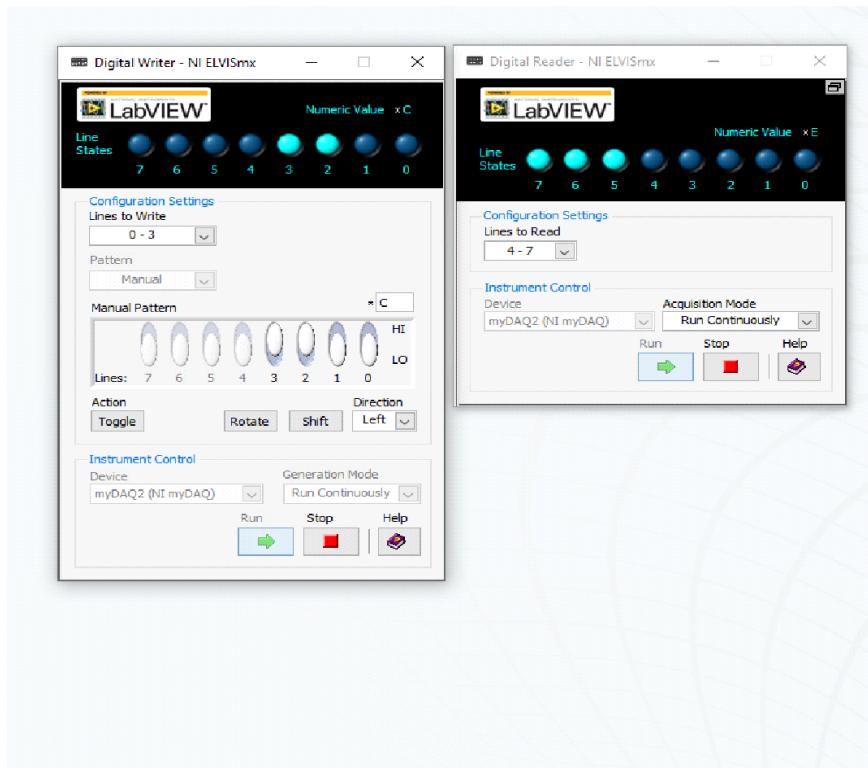

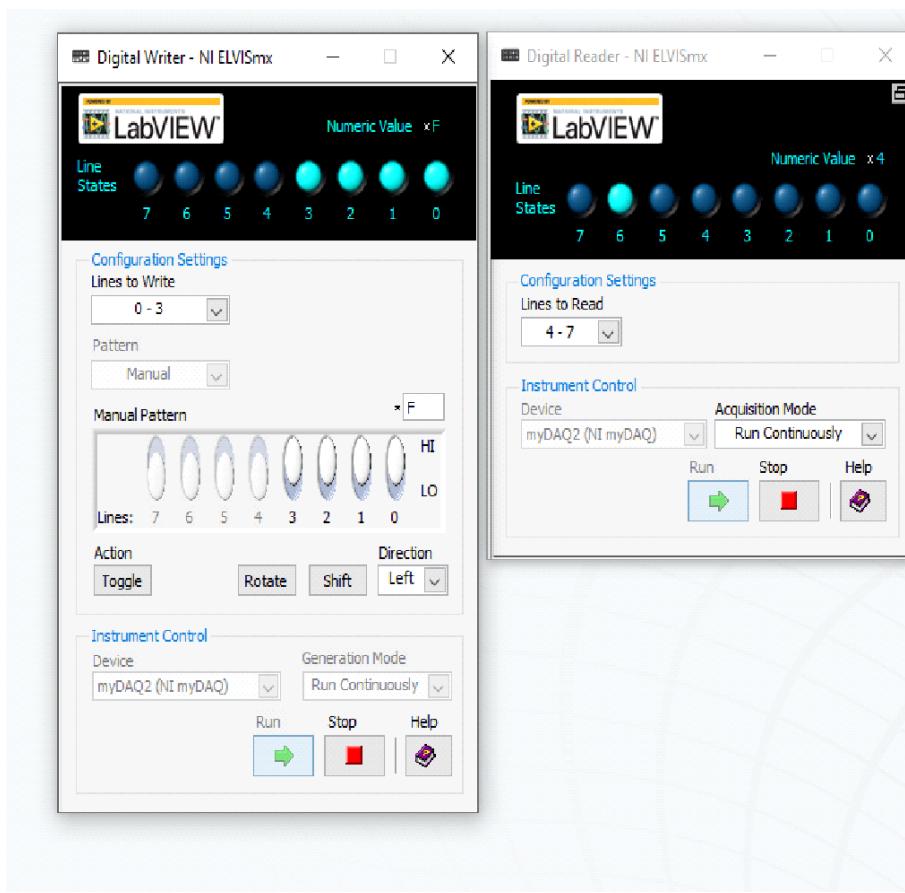



Result:

The realization of Binary to Gray Code Converter is done.

EXPERIMENT-3 (B)

Aim:

Design and implement Code converter- BCD to Excess-3

Requirements:

NI LabVIEW tool

Theory:

Describe the Binary Coded Decimal (BCD) number system and Excess-3 code in brief. And explain the method to convert the BCD to its equivalent Excess-3 code with an example. Also draw truth table for the same.

Binary Coded Decimal (BCD):

Numeric codes represent numeric information i.e. only numbers as a series of 0's and 1's. Numeric codes used to represent decimal digits are called Binary Coded Decimal (BCD) codes. A BCD code is one, in which the digits of a decimal number are encoded-one at a time into group of four binary digits. There are a large number of BCD codes in order to represent decimal digits 0, 1, 2, ..., 9, it is necessary to use a sequence of at least four binary digits. Such a sequence of binary digits which represents a decimal digit is called code word.

Excess-3 Code:

It is a non-weighted code. It is also a self-complementing BCD code used in decimal arithmetic units. . The Excess-3 code for the decimal number is performed in the same manner as BCD except that decimal number 3 is added to the each decimal unit before encoding it to binary.

BCD to Excess-3:

To convert from binary code A to binary code B, the input lines must supply the bit combination of elements as specified by code A and the output lines must generate the corresponding bit combination of code B. A combinational circuit performs this transformation by means of logic gates. As we want to design 4-bit code, we must use four input variables and four output variables. Designate the four input binary variables by the symbols B₀, B₁, B₂ and B₃, and the four output variables by E₀, E₁, E₂ and E₃. The truth table relating the input and output variables is as shown. A two-level logic diagram may be obtained directly from the Boolean expressions derived by the maps. The expressions obtained may be manipulated for the purpose of using common gates for two or more outputs. This manipulation illustrates flexibility obtained with multiple-output systems when implemented with three or more levels of gates.

Circuit Diagram:

Mathematical equation :

$$E_0 = B_0$$

$$E_1 = B_1 B_0 + B'_1 B'_0 = B_1 B_0 (B_1 B_0)'$$

$$\begin{aligned} E_2 &= B'_2 B_1 + B'_2 B_0 + B_2 B'_1 B'_0 \\ &= B'_2 (B_1 + B_0) \end{aligned}$$

$$E_2 = B'_2 (B_1 + B_0) + B_2 (B_1 + B_0)'$$

$$\begin{aligned} E_3 &= B'_2 (B_1 + B_0) + B_2 (B_1 + B_0)' \\ &= B_2 + B_2 B_1 + B_2 B_0 \\ &= B_3 + B_2 (B_1 + B_0) \end{aligned}$$

Circuit Diagram:

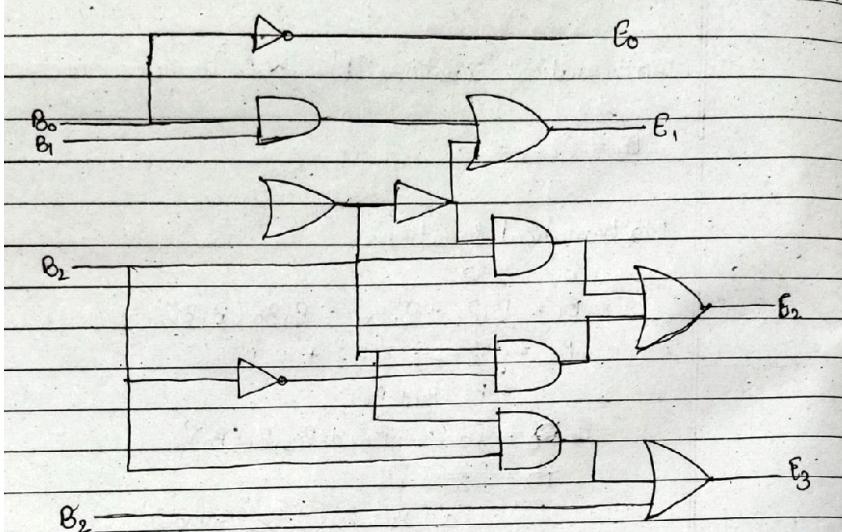


Fig: BCD TO EXCESS-3 code converter.

K-map for E₃

	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	x	x	x	x
10	1	1	x	x

K-map for E₂

	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	x	x	x	x
10	0	1	x	x

K-map for E₁

	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	x	x	x	x
10	1	0	x	x

K-map for E₀

	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	x	x	x	x
10	1	0	x	x

Observation Table:

Input Variables- B_3, B_2, B_1, B_0



Output Variables- E_3, E_2, E_1, E_0


Where B_3, B_2, B_1, B_0 represents the bits of BCD code,


E_3, E_2, E_1, E_0 represents the bits of Excess-3 code.

Input (BCD Code)				Output (Excess-3 Code)			
B_3	B_2	B_1	B_0	E_3	E_2	E_1	E_0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Output:

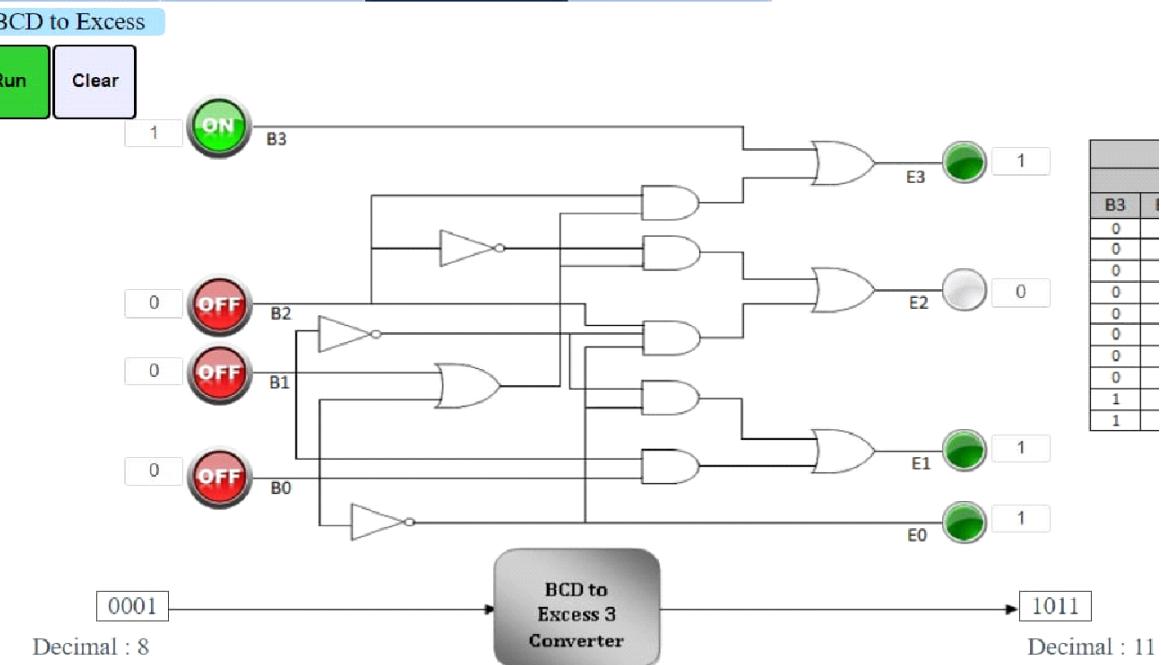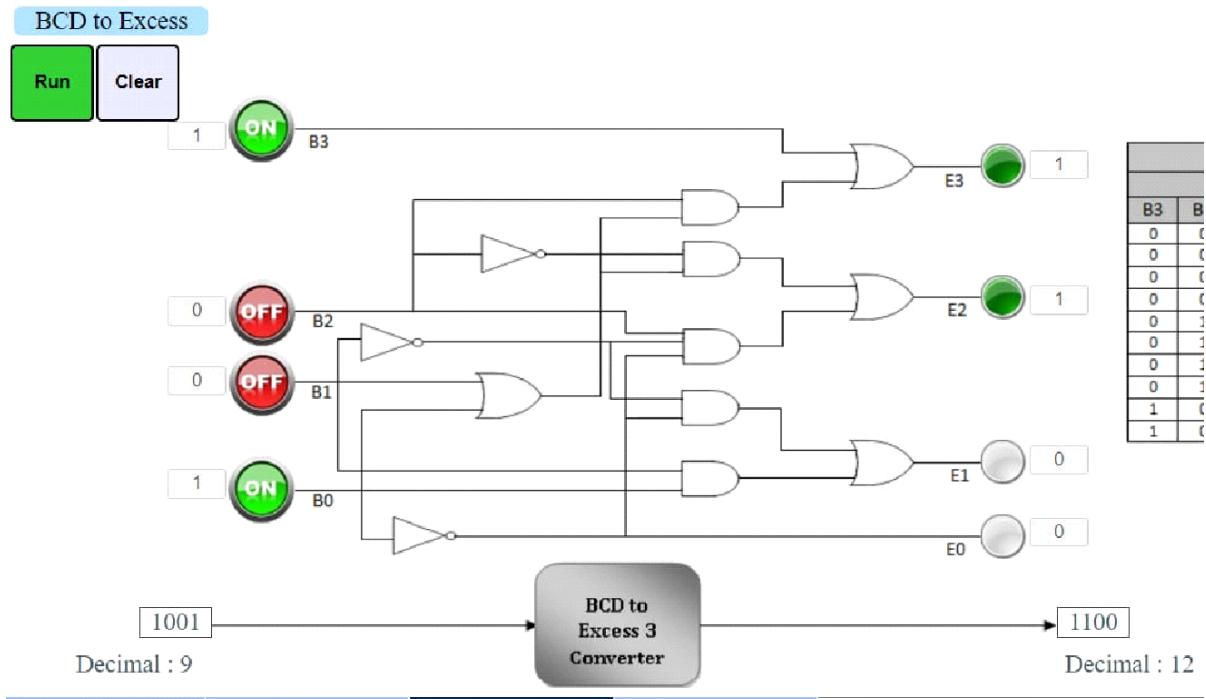

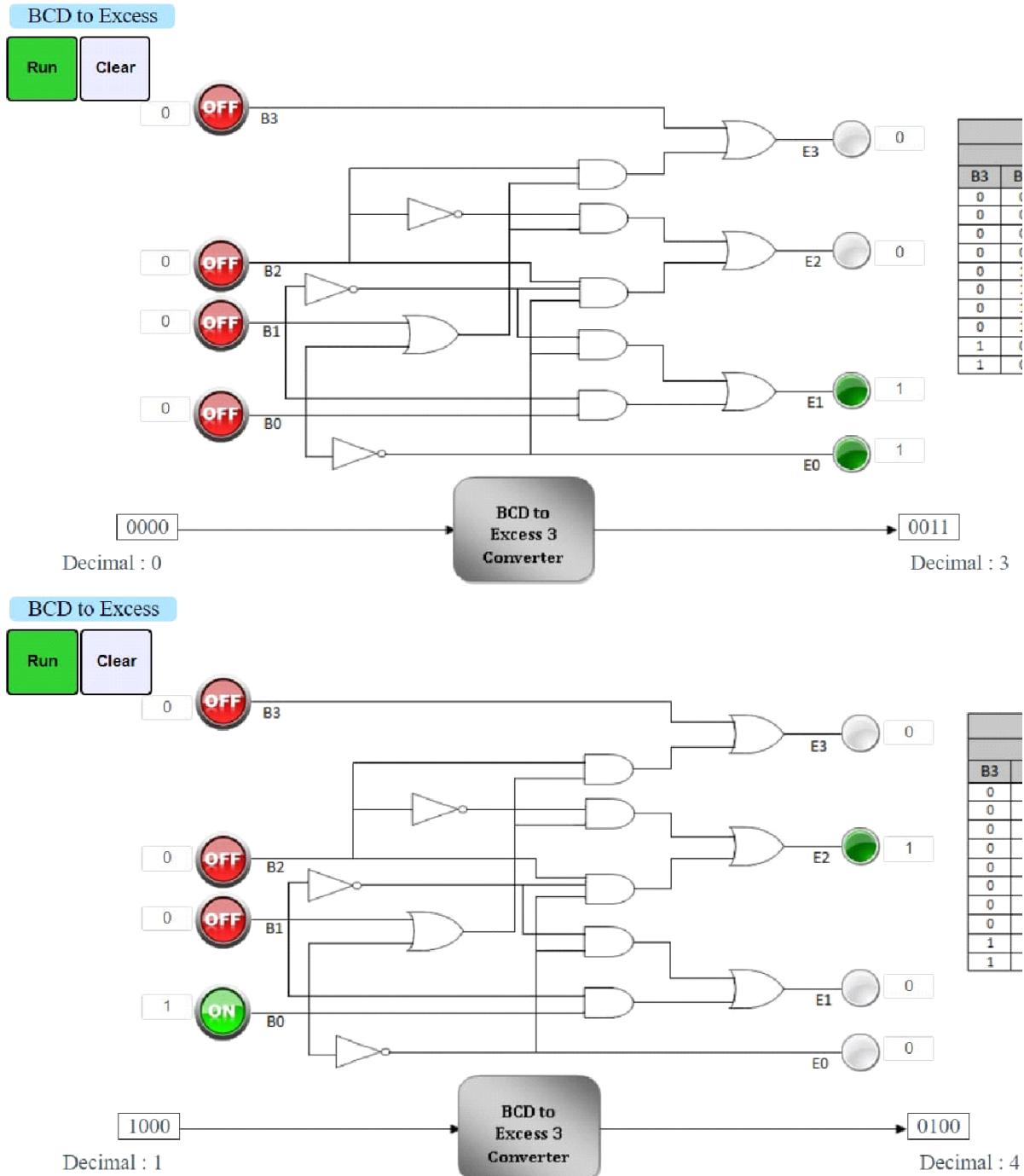

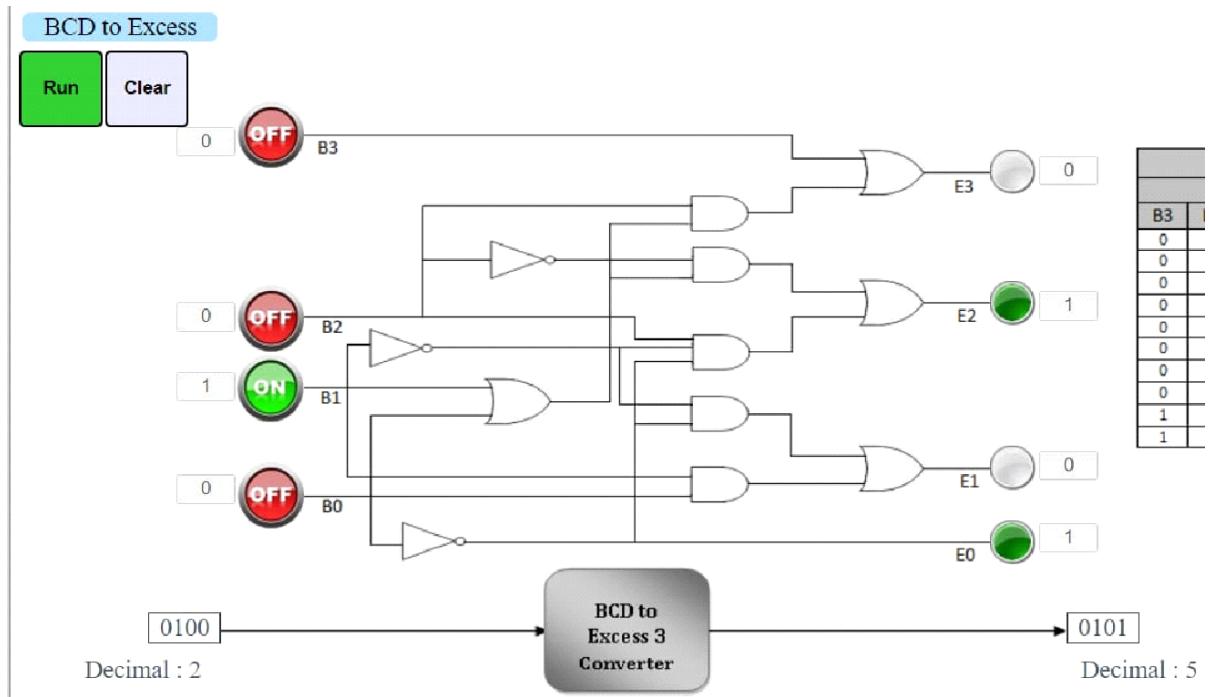

Result:

The realization of BCD to Excess-3 Code Converter is done.

Note: The whole documentation is to be converted to pdf/word format before uploading it on the Moodle. Only the pdf/word format will be acceptable. The Submission has to be done on time. After the deadline no submission of the particular experiment will be acceptable.